


NT Assignment - 2

NAME : ADITI ROUT

ID : B120003

BRANCH : CSE

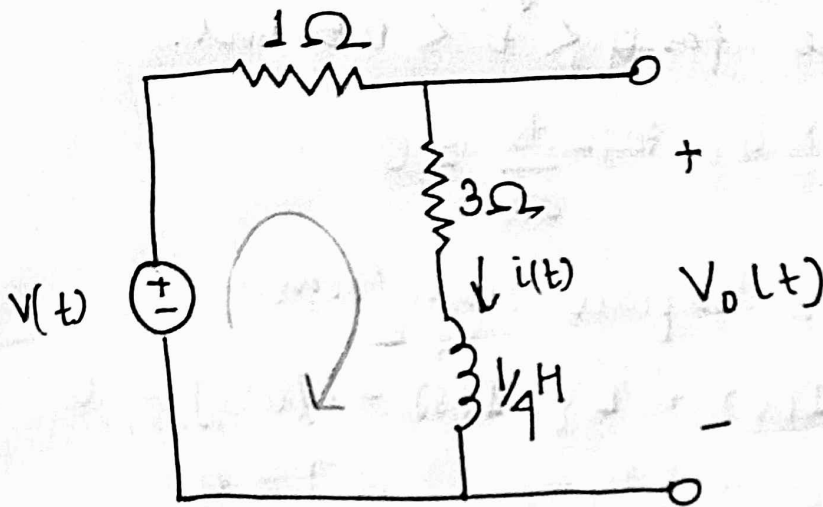Q1. consider given circuit : Find $V_o(t)$ if $i(0) = 2$ A and $v(t) = 0$



$$i(t) = i(0) e^{-t/\tau}$$

$$R_{eq} = 3\Omega + 1\Omega = 4\Omega$$

$$\tau = L/R_{eq} = \frac{1/4}{4} = \frac{1}{16}$$

$$i(t) = 2e^{-16t}$$

$$V_o(t) = 3i + L \frac{di}{dt} = 6e^{-16t} + \frac{1}{4}(-16)2e^{-16t}$$


$$V_o(t) = -2e^{-16t} u(t) \text{ volts.}$$

Q2. $v(t) = 20e^{-10^3 t} \text{ V}, t > 0$

$i(t) = 4e^{-10^3 t} \text{ mA}, t > 0$ $i(0) = 4 \text{ mA}$

a) Find R , L , & τ .

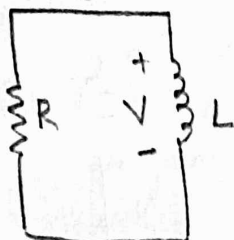b) Calculate the energy dissipated in resistance for $0 < t < 0.5 \text{ ms}$.



a) $Ri(t) + L \frac{di}{dt} = 0$

Use Laplace transform.

$$RI(s) + L[sI(s) - i(0^+)] = 0$$

$$\Rightarrow RI(s) + L[sI(s) - 4] = 0$$

$$\Rightarrow I(s)[R + sL] = 4L$$

$$\Rightarrow I(s) = \frac{4L}{R + sL}$$

$$I(s) = \frac{4}{\frac{R}{L} + s}$$

Using inverse Laplace.

$$i(t) = 4e^{-\frac{R}{L}t} \text{ mA}$$

From comparing eqⁿs we get.

$$\frac{R}{L} = \frac{1}{\tau} = 10^3 \Rightarrow \boxed{\tau = 1 \text{ ms}}$$

We know.

$$i(t) = \frac{V(t)}{R} \Rightarrow \boxed{R = 5 \text{ k}\Omega}$$

and so $\frac{R}{L} = 10^3$

$$\Rightarrow L = \frac{5 \times 10^3}{10^3} = 5 \text{ H}$$


$$\boxed{\therefore L = 5 \text{ H}, R = 5 \text{ k}\Omega, \tau = 1 \text{ ms}}$$

b) Energy dissipated in the resistor is

$$\begin{aligned} \mathcal{E} &= \int_0^t P dt = \int_0^t 80 \times 10^{-3} e^{-2 \times 10^3 t} dt \\ &= \left[-\frac{80 \times 10^{-3}}{2 \times 10^3} e^{-2 \times 10^3 t} \right]_0^{0.5 \times 10^{-3}} \\ &= 40(1 - e^{-1}) \mu J \\ &= 25.28 \mu J \end{aligned}$$

(Ans)

3Q Find the time constant of circuit.

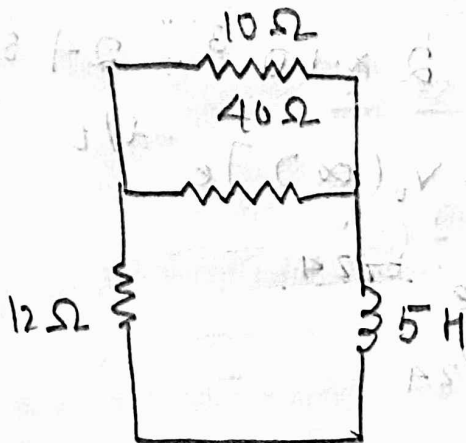


$$R_{eq} = \frac{10 \times 40}{40 + 10} + 12$$

$$= 8 + 12 = 20 \Omega$$

$$L = 5 \text{ H}$$

$$\tau = \frac{L}{R} = \frac{5}{20} = 0.25 \text{ s}$$

(a)

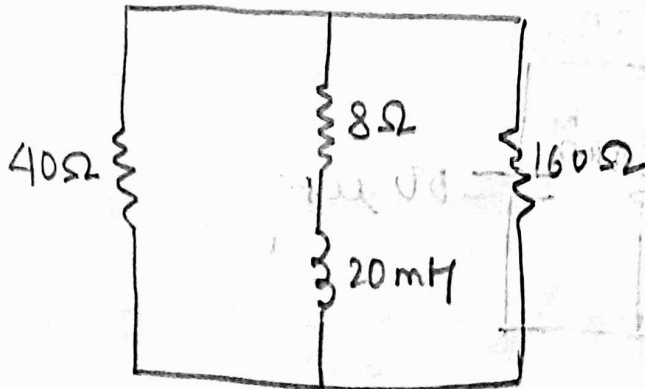


(b)

$$R_{eq} = \frac{40 \times 160}{200} + 8 = 40 \Omega$$

$$\tau = \frac{L}{R} = \frac{20 \times 10^{-3}}{40} = 0.5 \text{ ms}$$

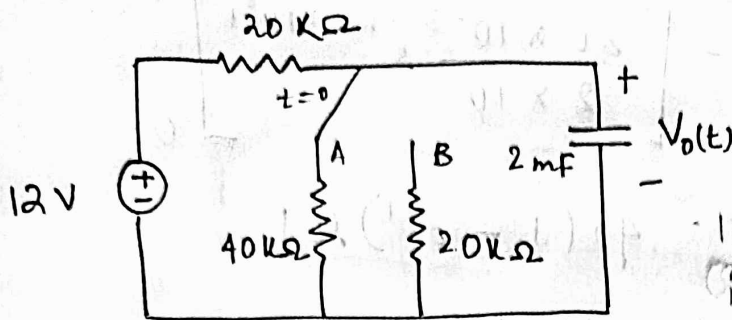4Q Assuming the switch in fig has been in position A for a long time and is moved to position B at $t = 0$, find $V_o(t)$ for $t \geq 0$.



Initially,

$$I = \frac{12}{20+40} = 0.2 \times 10^{-3} \text{ A}$$

So

$$V = 12 - (20 \times 10^3 \times 0.2 \times 10^{-3})$$

$$= 12 - 4 = 8 \text{ V}$$

So

$$Q_0 = CV = 8 \times 2 \times 10^{-3} = 16 \times 10^{-3} \text{ C}$$

When the switch is at position B, the circuit reaches steady state, by voltage division.

$$V_o(\infty) = \frac{30}{30+20} (12 \text{ V}) = 7.2 \text{ V}$$

$$R_{th} = 20 \parallel 30 = \frac{20 \times 30}{50} = 12 \text{ k}\Omega$$


$$\tau = R_{th}C = 12 \times 10^3 \times 2 \times 10^{-3} = 24 \text{ sec}$$

$$V_o(t) = V_o(\infty) + [V_o(0) - V_o(\infty)]e^{-t/\tau}$$

$$= 7.2 + (8 - 7.2)e^{-t/24}$$

$$= 7.2 + 0.8e^{-t/24}$$

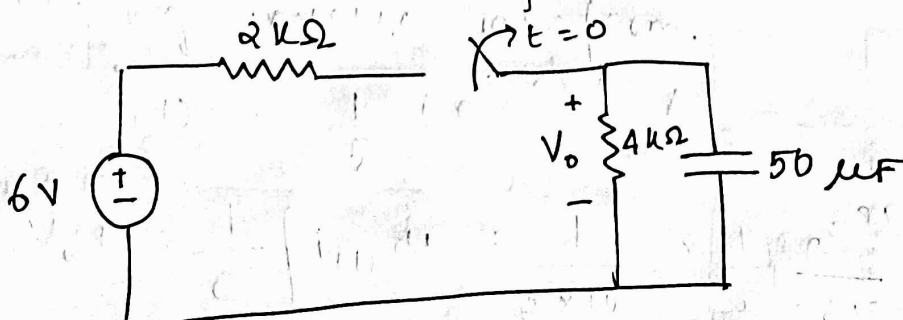Q5. The switch in the given figure opens at $t = 0$. Find V_o for $t > 0$.



For $t < 0$, the switch is closed so that

$$V_0(0) = \frac{4}{2+4}(6) = 4 \text{ V.}$$

For $t > 0$, we have source-free RC circuit

$$\begin{aligned} \tau = RC &= 50 \times 10^{-6} \times 6 \times 10^3 \\ &= 300 \times 10^{-3} \\ &= 3 \times 10^2 \times 10^{-3} = 3 \times 10^{-1} = 0.3 \text{ sec} \end{aligned}$$

$$\begin{aligned} \text{So } V_0(t) &= V_0(0) e^{-t/\tau} \\ &= 4 e^{-t/0.3} = 4 e^{-10/3 t}. \end{aligned}$$

Q6. A circuit is described by $4 \frac{dv}{dt} + v = 10$

a) What is the time constant of the circuit?

b) What is $V(\infty)$, the final value of v ?

c) If $V(0) = 2$, find $V(t)$ for $t \geq 0$.

$$\text{Let } V = V_n + V_p, \text{ where } V_p = 10$$

$$\text{So } V_n = \frac{1}{4} V_n e^{-t/4} \text{ and, } V_n = 4e$$

$$\text{So, } V = 10 + 4e^{-0.25t}$$

$$\text{It is given } V(0) = 2$$
$$\Rightarrow 10 + A = 2$$
$$\Rightarrow A = -8.$$

$$\text{So } \boxed{V = 10 - 8e^{-0.25t}} \dots (i)$$

$$\text{a) time constant} = \tau = \frac{100}{25} = 4 \text{ sec.}$$

$$\text{b) } V(\infty) = 10 \text{ V from eq}^n (i)$$

$$\text{c) If } V(0) = 2.$$

$$\text{then } \boxed{V(t) = 10 - 8e^{-0.25t} \quad u(t) \text{ V}}$$

Q To find Laplace transforms of following.

Q1. $(t^2 + 1)^2$

Solⁿ Let $f(t) = (t^2 + 1)^2$

$$\begin{aligned}\text{Now } L\{f(t)\} &= L\{(t^2 + 1)^2\} \\ &= L\{t^4 + 2t^2 + 1\} \\ &= L\{t^4\} + 2L\{t^2\} + L\{1\} \\ &= \frac{4!}{s^4} + 2 \cdot \frac{2!}{s^3} + \frac{1}{s} \quad (\text{Ans})\end{aligned}$$

Q2. $(\sin t + \cos t)^2$

Solⁿ Let $f(t) = (\sin t + \cos t)^2$

$$\begin{aligned}&= \sin^2 t + \cos^2 t + 2\sin t \cos t \\ &= 1 + \sin 2t \quad [\because \sin 2t = 2\sin t \cos t]\end{aligned}$$

$$\begin{aligned}\text{Now } L\{f(t)\} &= L\{1 + \sin 2t\} \\ &= L\{1\} + L\{\sin 2t\} \\ &= \frac{1}{s} + \frac{2}{s^2 + 4} \\ &= \frac{s^2 + 4 + 2s}{s(s^2 + 4)} \quad (\text{Ans})\end{aligned}$$

Q3. $\cos^3 2t$

Solⁿ Let $f(t) = \cos^3 2t$

So $\cos 6t = \cos 3(2t)$

$$= 4\cos^3 2t - 3\cos 2t$$

$$\therefore 4\cos^3 2t = \cos 6t + 3\cos 2t$$

[we know
 $\cos 3A = 4\cos^3 A - 3\sin A$]

$$\Rightarrow \cos^3 2t = \frac{1}{4} (\cos 6t + 3 \cos 2t)$$

$$\text{Now } L\{\cos^3 2t\} = \frac{1}{4} L\{\cos 6t\} + \frac{3}{4} L\{\cos 2t\}$$

[by linearity property]

$$= \frac{1}{4} \left(\frac{s}{s^2+36} \right) + \frac{3}{4} \left(\frac{s}{s^2+4} \right)$$

$$= \frac{s}{4} \left[\frac{1}{s^2+36} + \frac{3}{s^2+4} \right]$$

(Ans)

Q To find Inverse Laplace Transform of following.

Q4. $\frac{s}{(s^2+a^2)^2}$

Soln.

Let $f(s) = \frac{s}{(s^2+a^2)^2}$

Taking Inverse Laplace transform on both sides.

$$L^{-1}\{f(s)\} = L^{-1}\left\{\frac{s}{(s^2+a^2)^2}\right\}$$

$$= L^{-1}\left\{\frac{-1}{2} \frac{d}{ds}\left(\frac{1}{s^2+a^2}\right)\right\}$$

By inverse Laplace transform of derivative,

$$\text{If } L^{-1}\{f(s)\} = f(t)$$

$$\text{then } L^{-1}\left\{\frac{d}{ds} f(s)\right\} = -t f(t)$$

$$\begin{aligned}
 \therefore \mathcal{L}^{-1} \left\{ -\frac{1}{2} \frac{d}{ds} \left(\frac{1}{s^2 + a^2} \right) \right\} &= -\frac{1}{2} \mathcal{L}^{-1} \left\{ \frac{d}{ds} \left(\frac{1}{s^2 + a^2} \right) \right\} \\
 &= -\frac{1}{2} (-1) t \mathcal{L}^{-1} \left\{ \frac{1}{s^2 + a^2} \right\} \\
 &= \frac{1}{2} t \cdot \frac{1}{a} \sin at.
 \end{aligned}$$

$$\boxed{\mathcal{L}^{-1} \{ f'(s) \} = \frac{t \sin at}{2a}}$$

Q5: $Y(s) = \frac{1}{s(s-1)}$

Soln.

Let $y(t)$ be inverse Laplace transform of $Y(s)$.

$$y(0) = \lim_{s \rightarrow 0} s Y(s)$$

$$Y(s) = \frac{1}{s(s-1)} = \frac{A}{s} + \frac{B}{s-1}$$

$$= \frac{A(s-1) + Bs}{s(s-1)}$$

So Now $A = -1$ at $s = 0$

$B = 1$ at $s = 1$.

$$Y(s) = -\frac{1}{s} + \frac{1}{s-1}$$


\Downarrow

$$\boxed{y(t) = -u(t) + e^t u(t)} \quad (\text{Ans}).$$

RL and RC Network:

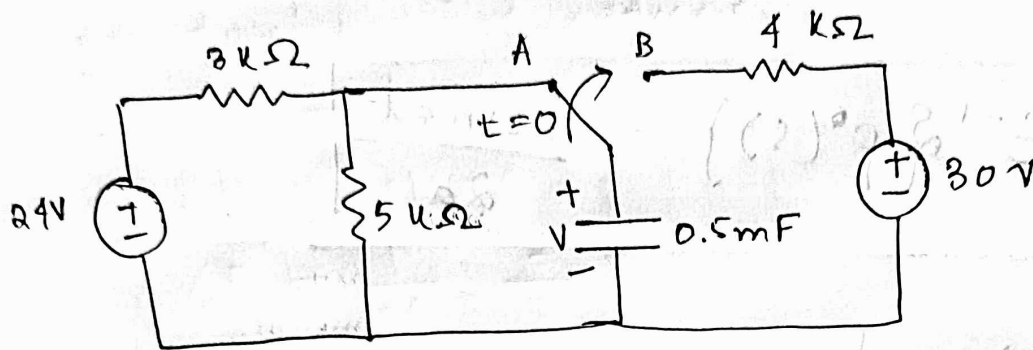Q1.

The switch in the figure has been in position A for a long time. At $t=0$, the switch moves to B. Determine $V(t)$ for $t>0$ and calculate its value at $t=1s$ & $4s$.



For $t < 0$, the switch is at position A. Since V is the same as the voltage across the $5k\Omega$ resistor, the voltage across the capacitor just before $t=0$ is obtained by voltage division as

$$V(0^-) = \frac{5}{5+3} (24) = 15V.$$

$$V(0^-) = V(0) = V(0^+) = 15V.$$

For $t > 0$, $R_{th} = 4k\Omega$

$$\tau = R_{th}C = 4 \times 10^3 \times 0.5 \times 10^{-3} = 2s.$$

Since capacitor acts like an open circuit to dc at steady state, $V(\infty) = 30V$. Thus,

$$\begin{aligned} V(t) &= V(\infty) + [V(0) - V(\infty)]e^{-t/\tau} \\ &= 30 + (15 - 30)e^{-t/2} = (30 - 15e^{-0.5t})V \end{aligned}$$


At $t=1$,

$$V(1) = 30 - 15e^{-0.5} = 20.902V$$

At $t=4$,

$$V(4) = 30 - 15e^{-2} = 27.77V.$$

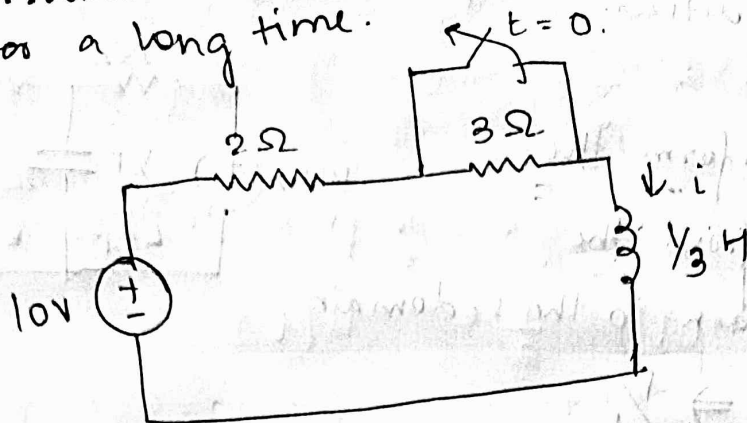Q2. Find $i(t)$ in the circuit in the figure. Assume that the switch has been closed for a long time.



When $t < 0$, $3\text{-}\Omega$ resistor is short-circuited, & the inductor acts like a short circuit. The current through the inductor at $t = 0^-$

$$i(0^-) = \frac{10}{2} = 5 \text{ A.}$$

Since the inductor current cannot change instantaneously,

$$i(0) = i(0^+) = i(0^-) = 5 \text{ A.}$$

When $t > 0$, the switch is open. The $2\text{-}\Omega$ & $3\text{-}\Omega$ resistors are in series, so that

$$i(\infty) = \frac{10}{2+3} = 2 \text{ A.}$$

The Thevenin resistance across the inductor terminals is $R_{th} = 2 + 3 = 5 \Omega$.

For the time constant,

$$\tau = \frac{L}{R_{th}} = \frac{1/3}{5} = \frac{1}{15} \text{ s}$$

Thus,

$$\begin{aligned} i(t) &= i(\infty) + [i(0) - i(\infty)] e^{-t/\tau} \\ &= 2 + (5 - 2) e^{-15t} = 2 + 3e^{-15t} \text{ A, } t > 0. \end{aligned}$$


for $t > 0$, KVL must be satisfied.

$$10 = 5i + L \frac{di}{dt}$$

$$5i + L \frac{di}{dt} = [10 + 15e^{-15t}] + \left[\frac{1}{3}(3)(-15)e^{-15t} \right] = 10.$$

30 Find $V_o(t)$ in the circuit in fig, assuming zero initial condition.

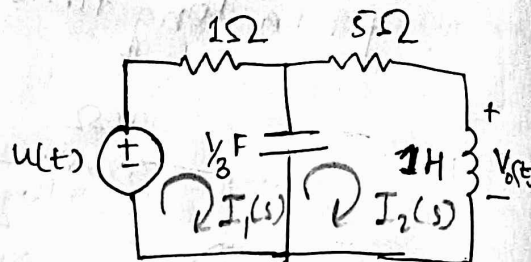We first transform the circuit from the time domain to the s-domain.



$$u(t) \Rightarrow \frac{1}{s}$$

$$1 \text{ H} \Rightarrow sL = s$$

$$\frac{1}{3} \text{ F} \Rightarrow \frac{1}{sC} = \frac{3}{s}$$

The resulting s-domain circuit in the fig.

Applying mesh analysis.

For mesh 1,

$$\frac{1}{s} = \left(1 + \frac{3}{s}\right) I_1 - \frac{3}{s} I_2 \quad (i)$$

For mesh 2,

$$0 = -\frac{3}{s} I_1 + \left(s + 5 + \frac{3}{s}\right) I_2$$

$$\therefore I_1 = \frac{1}{3} (s^2 + 5s + 3) I_2 \quad (ii)$$

From (i) & (ii)

$$\frac{1}{s} = \left(1 + \frac{3}{s}\right) \frac{1}{3} (s^2 + 5s + 3) I_2 - \frac{3}{s} I_2$$

Multiplying through by $3s$ gives

$$3 = (s^3 + 8s^2 + 18s) I_2 \Rightarrow I_2 = \frac{3}{s^3 + 8s^2 + 18s}$$

$$V_o(s) = s I_2 = \frac{3}{s^2 + 8s + 18} = \frac{3}{\sqrt{2}} \frac{\sqrt{2}}{(s+4)^2 + (\sqrt{2})^2}$$

Taking the inverse transform yields

$$V_o(t) = \frac{3}{\sqrt{2}} e^{-4t} \sin \sqrt{2} t \text{ V}, \quad t > 0$$

4Q The output of a linear system is ~~$y(t) = 10e^{-t} \cos 4t$~~
 $y(t) = 10e^{-t} \cos 4t u(t)$ when the input is
 $x(t) = e^{-t} u(t)$. Find the transfer function
of the system and its impulse response.

If $x(t) = e^{-t} u(t)$ and $y(t) = 10e^{-t} \cos 4t u(t)$,
then
 $X(s) = \frac{1}{s+1}$ and $Y(s) = \frac{10(s+1)}{(s+1)^2 + 4^2}$

Hence,

$$H(s) = \frac{Y(s)}{X(s)} = \frac{10}{(s+1)^2 + 16} = \frac{10}{s^2 + 2s + 17}$$


$$\Rightarrow H(s) = \frac{10}{4} \left(\frac{4}{(s+1)^2 + 4^2} \right)$$

so now

$$\boxed{h(t) = 2.5 e^{-t} \sin 4t} \quad (\text{Ans})$$

impulse response.

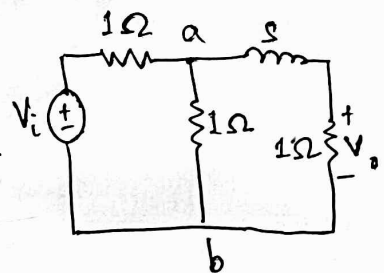5Q For the s-domain circuit in given figure.
Find a) the transfer function
 $H(s) = V_o/V_i$
b) the impulse response.



a) Using voltage division,

$$V_o = \frac{1}{s+1} V_{ab} \quad \dots (i)$$

$$\text{but } V_{ab} = \frac{1 \parallel (s+1)}{1 + 1 \parallel (s+1)} V_i = \frac{(s+1)/(s+2)}{1 + (s+1)/(s+2)} V_i$$

$$\text{or } V_{ab} = \frac{s+1}{2s+3} V_i \quad \dots (ii)$$

Substituting (ii) in (i) gives.

$$V_o = \frac{V_i}{2s+3}$$

Thus, impulse response is

$$H(s) = \frac{1}{2} \left(\frac{1}{s + \frac{3}{2}} \right) \quad \left[\because H(s) = \frac{V_o}{V_i} \right]$$

b) Its inverse l.T gives impulse response -

$$h(t) = \frac{1}{2} e^{-3t/2} u(t)$$