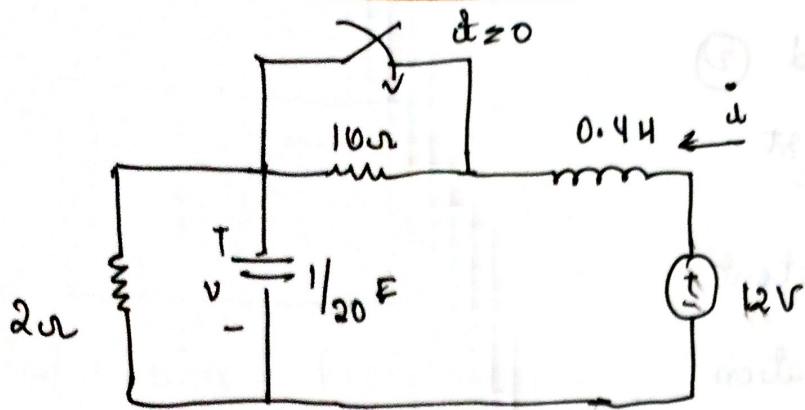


Q3
a)



$$(i) \quad i(0^+) = \frac{12}{10+2} = \frac{12}{12} = 1 \text{ A}.$$

$$V(0^+) = \frac{10}{12} \times 12 = 10 \text{ V}$$


$$(ii) \quad \frac{di}{dt}(0^+) = \frac{V}{L} = \frac{10}{0.4} = \frac{100}{4} = 25 \text{ A/s}.$$

$$\frac{dV}{dt}(0^+) = \frac{i_c(0^+)}{C} = 0 \text{ V/s}.$$

$$(iii) \quad i(\infty) = \frac{12}{12} = 1 \text{ A}.$$

$$V(\infty) = 12 \text{ V}.$$

(b)

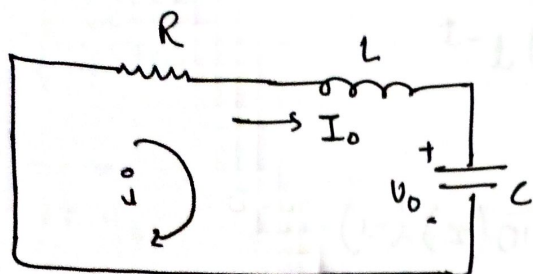

Consider series RLC circuit. The circuit is being excited by energy initially stored in capacitor & inductor. The energy is represented by initial capacitor voltage V_0 & initial inductor current.

I_0 . Thus, at $t = 0$,

$$V(0) = \frac{1}{C} \int_{-\infty}^0 i dt = V_0$$

$$i(0) = I_0 \quad \text{--- (1)}$$

Apply KVL around the loop

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_{-\infty}^t i(\tau) d\tau = 0$$

differentiate w.r.t t

$$\frac{d^2 i}{dt^2} + \frac{C}{L} \frac{di}{dt} + \frac{i}{LC} = 0$$

This second order differential eq. is reason for calling RLC circuit an IIR. To solve such a second order equation, we require 2 initial conditions such as initial value of i and its first derivative or initial values of some i & V .

$$Ri(0) + L \frac{di}{dt}(0) + V_0 = 0$$

$$\text{or } \frac{di(0)}{dt} = -\frac{1}{L} (RI_0 + V_0) \quad \text{--- (2)}$$

Ragini Sharma
B120062

From eq ① and ②

$$\ddot{i} = A e^{st}$$

A and s \rightarrow constant

By differentiation

$$A s^2 e^{st} + \frac{AR}{L} s e^{st} + \frac{A}{LC} e^{st} = 0$$

$$A e^{st} \left(s^2 + \frac{Rs}{L} + \frac{1}{LC} \right) = 0$$

$$\text{So, } s^2 + \frac{Rs}{L} + \frac{1}{LC} = 0$$

↓
Characteristic equation

The two roots are \rightarrow

$$s_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_2 = \frac{-R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

A more compact way of expressing roots

$$s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2} \quad s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$


Now s_1 & $s_2 \rightarrow$ are natural frequencies
we get.

$$i_1 = A_1 e^{s_1 t}, \quad i_2 = A_2 e^{s_2 t}$$


$$\text{So, } i(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

i) if $\alpha > \omega_0$
 $\Rightarrow C > \frac{4L}{R^2}$

overdamped case

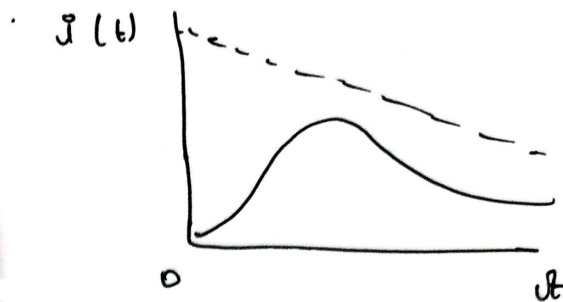

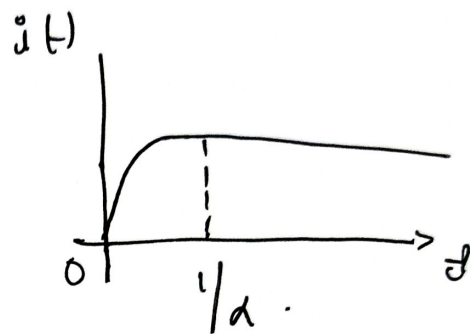ii) if $\alpha = \omega_0$,
 critically damped case
 $C = \frac{4L}{R^2}$



iii) if $\alpha < \omega_0$.
 underdamped case
 so, $C < \frac{4L}{R^2}$

